

Chapter 21

Chapter 21

Current & Charge


Electric Current

is a flow of electric charge

$$Q = It$$

$$1 \text{ A} = 1 \text{ C s}^{-1}$$



In a metal **electrons move**

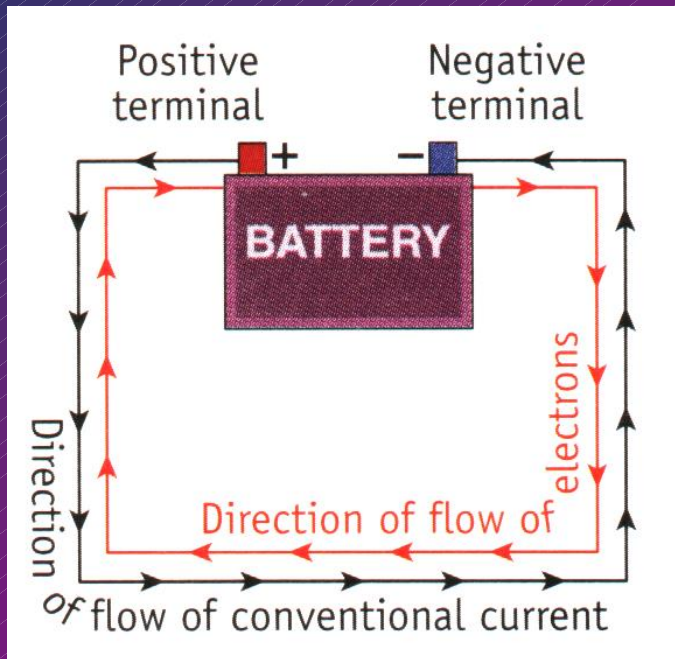


Electron flow
Conventional current

Direct Current (d.c.)


Alternating Current (a.c.)

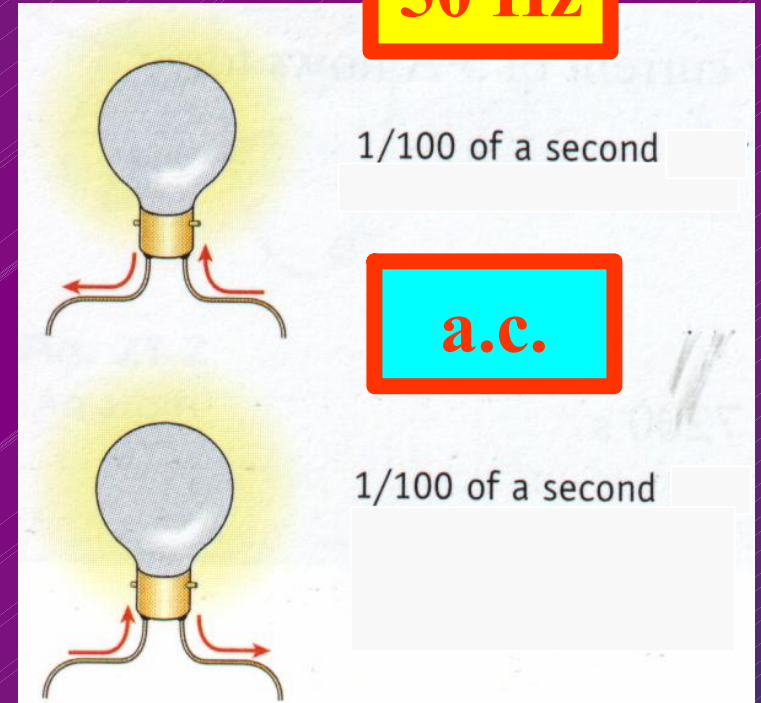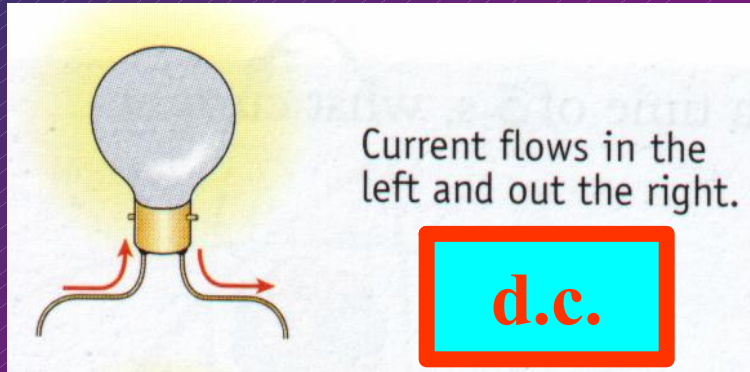

Current In A Series Circuit

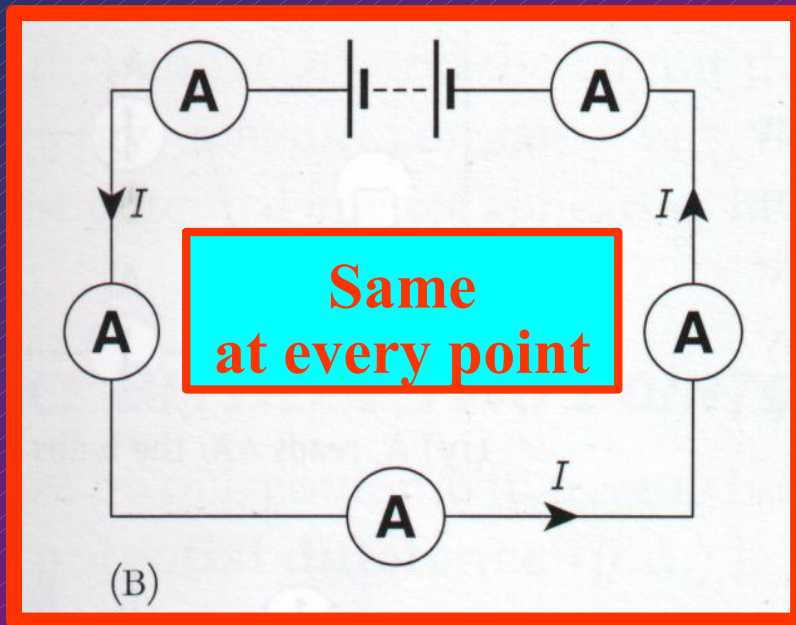


Current In Parallel Circuits

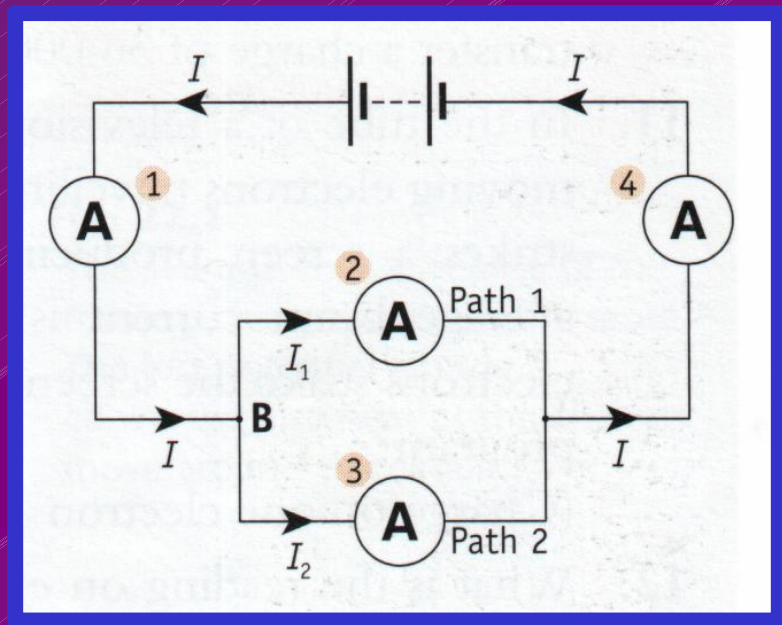

$$I = I_1 + I_2$$

Effects Of Electric Current

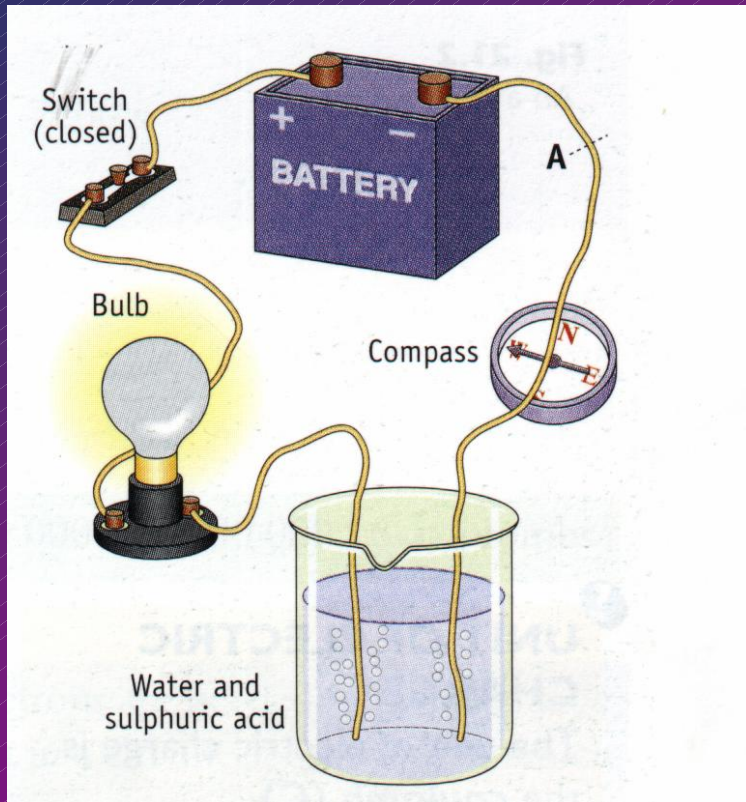

- **Heating**
- **Chemical**
- **Magnetic**

Chapter 22


Chapter 22

Electromotive Force


&

Potential Difference

Potential Difference (Voltage)

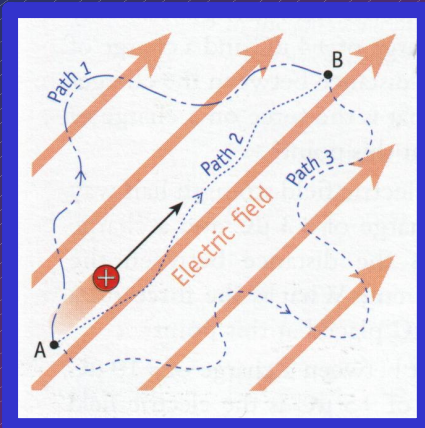

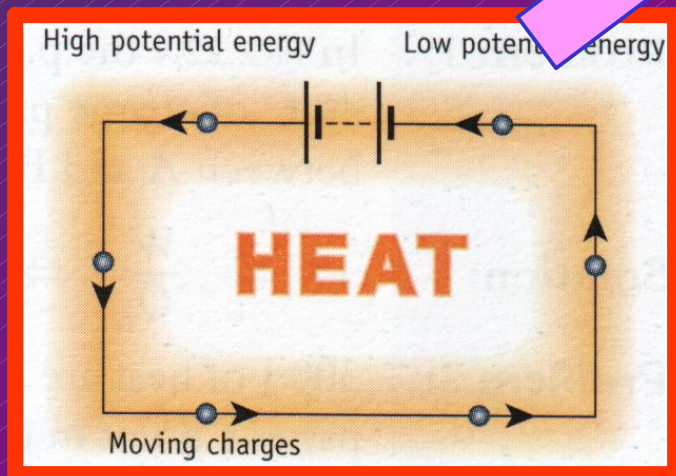**Work done
to move 1 C
from one point to another**



**Energy lost
by 1 C
as it moves from one point to another**

Potential Difference

$$V = \frac{W}{Q}$$

W = work / energy

V = potential difference (voltage)

Q = charge

$$\rightarrow W = VQ$$

$$= V(It)$$

$$\Rightarrow W = VIt$$

$$\frac{W}{t} = \frac{VIt}{t}$$


$$P = VI$$

Problem 1 The *pd* between A and B is 20 V. In a certain time 40 C of charge pass A. How much heat energy is produced between A and B?

$$V = W/Q$$

$$\rightarrow W = VQ$$

$$= 20 \times 40 = 800 \text{ J}$$

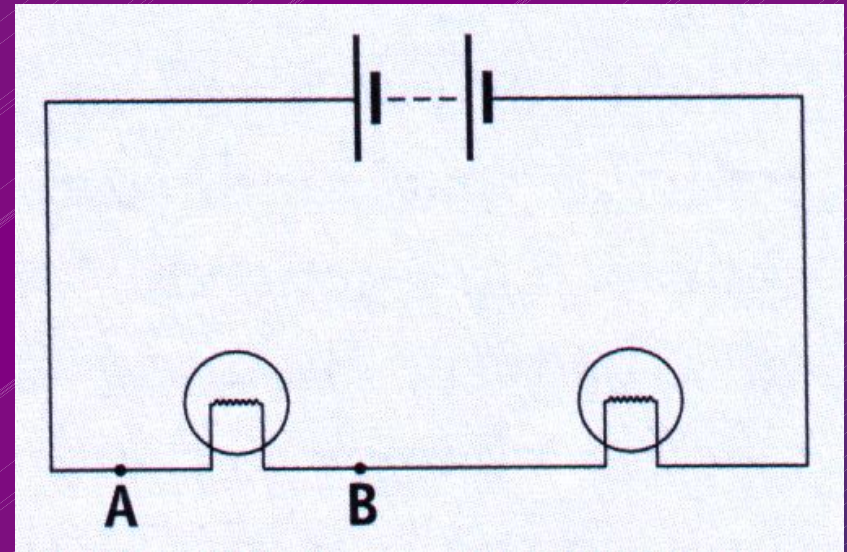


Problem 3 The current in a bulb is **2 A** when the *pd* across it is **230 V**. What is the power dissipated in the bulb?

$$P = VI$$

$$= (230)(2) = 460 \text{ W}$$


Voltages In Series And Parallel

Series

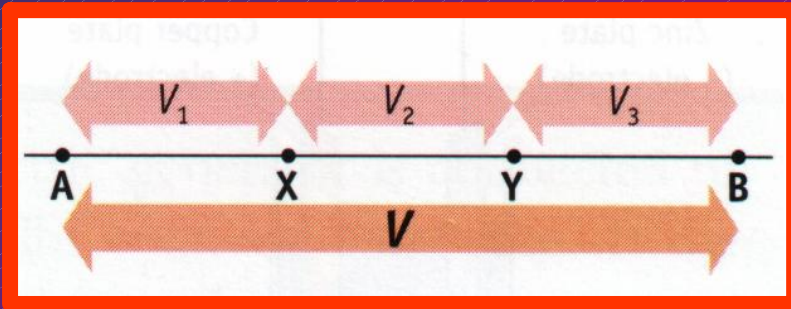

$$V = V_1 + V_2 + V_3$$


Parallel

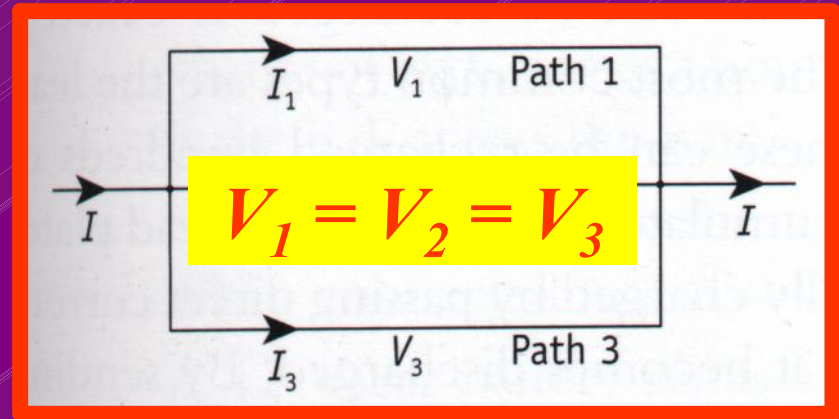

Same V

Ammeter

Voltmeter

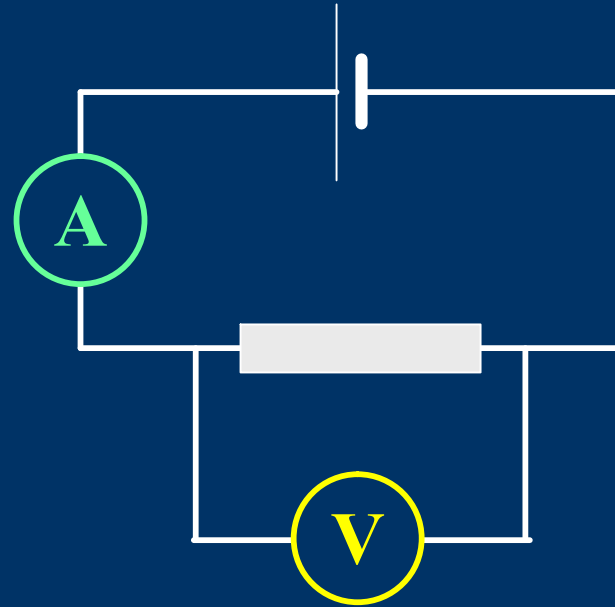

Electromotive Force

emf

The voltage
applied to a full circuit.

Symbol *E*

Unit Volt

Sources Of EMF

Cells

Simple Cell

$$E = 1.1 \text{ V}$$

Lead-Acid
Accumulator

$$E = 2 \text{ V}$$

Nickel Cadmium

$$E = 1.2 \text{ V}$$


Dry Cell

$$E = 1.5 \text{ V}$$

Nickel Metal Hydride


$$E = 1.2 \text{ V}$$

Primary & Secondary
Cells

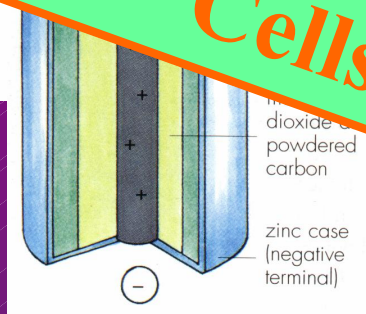

Sources Of EMF

Thermocouple

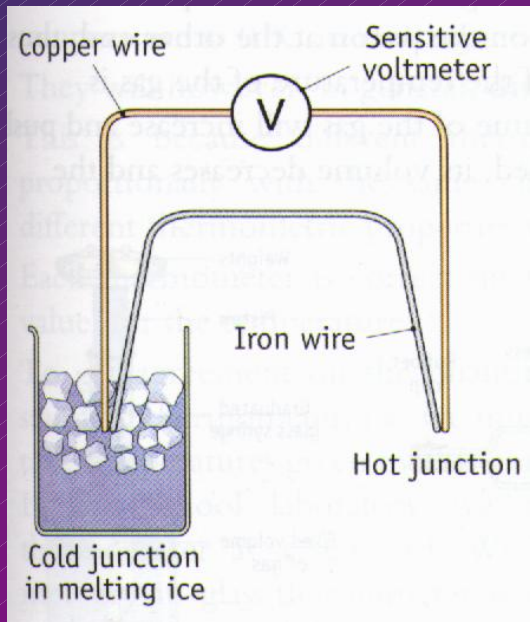

Mains

a.c.

$$E = 230 \text{ V}$$

50 Hz

Cells In Series

